

Key Design Points

- For nominal under-voltage set point V_{UV} :
 $R1 = (V_{UV} - 2.35 \text{ V}) / 50 \mu\text{A}$. $V_{OV} = (R1 \times 135 \mu\text{A}) + 2.5 \text{ V}$.
- Select C9 such that the core resets at V_{UV} and the DRAIN voltage $\leq 170 \text{ V}$ at V_{OV} . To reduce leakage spike, C8 may be added, adjusting C9 accordingly.
- Zener VR1 safely limits the DRAIN voltage below BV_{DSS} and guarantees transformer reset.
- Opto U2 should have a CTR of between 100% and 200% for optimum loop stability.
- At zero load, maximum input voltage, the bias voltage across C4 should be $\geq 8 \text{ V}$ (12 V to 15 V under nominal conditions).

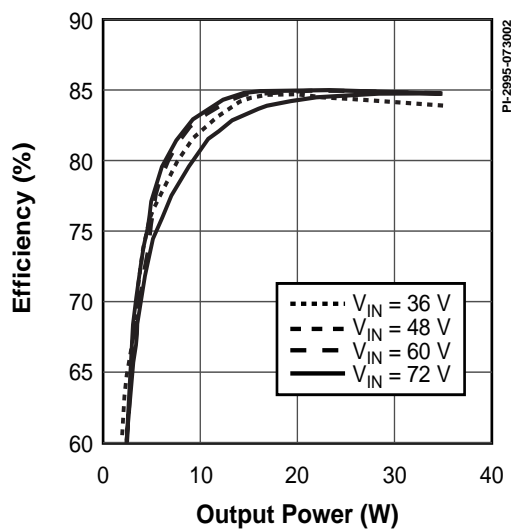


Figure 2. Efficiency vs. Output Power.

- Good layout practices should be followed:
 - Locate C5, C6 and R4 close to U1, with grounds returned to the SOURCE pin.
 - Primary return should be connected to the *DPA-Switch* tab, not the SOURCE pin.
 - Minimize the primary and secondary loop areas to reduce parasitic leakage inductance.
- Consult AN-31 and EPR-21 for additional design tips and information.

TRANSFORMER PARAMETERS	
Core	PR1408 Siemens N87 material, ungapped
Bobbin	P1408 8 pin (B&B B-096 or equivalent)
Winding Details	Primary: 7T + 8T, 27 AWG Secondary: 4T x 27 AWG
Winding Order (pin numbers)	Primary (4-3), tape, Secondary (5,6-7,8), Tape, Primary (3-1), tape
Inductance	Primary: 450 $\mu\text{H} \pm 25\%$, Leakage 1 μH (max)
Primary Resonant Frequency	3.8 MHz (minimum)

Table 1. Transformer Construction Information.

OUTPUT INDUCTOR PARAMETERS	
Core	PR1408 Siemens N87 material Gap for A_L of 163 nH/T ²
Bobbin	P1408 8 pin (B&B B-096 or equivalent)
Winding Details	Bias: 18T, 32 AWG, Main: 7T, 2x24 AWG
Winding Order (pin numbers)	Bias (1-2), tape, Main winding (7,8-5,6), tape
Inductance Pins 5,6-7,8	8 $\mu\text{H} \pm 10\%$

Table 2. Output Inductor Construction Information.

For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, **TOPSwitch**, **TinySwitch** and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** is a trademark of Power Integrations, Inc. ©Copyright 2002, Power Integrations, Inc.

WORLD HEADQUARTERS AMERICAS

Power Integrations, Inc.
San Jose, CA 95138 USA
Customer Service:
Phone: +1 408-414-9665
Fax: +1 408-414-9765
e-mail: usasales@powerint.com

CHINA

Power Integrations International Holdings, Inc.
China
Phone: +86-755-8367-5143
Fax: +86-755-8377-9610
e-mail: chinasales@powerint.com

EUROPE & AFRICA

Power Integrations (Europe) Ltd.
United Kingdom
Phone: +44-1344-462-300
Fax: +44-1344-311-732
e-mail: eurosales@powerint.com

KOREA

Power Integrations
International Holdings, Inc.
Seoul, Korea
Phone: +82-2-782-2840
Fax: +82-2-782-4427
e-mail: koreasales@powerint.com

SINGAPORE

Power Integrations, Singapore
Republic of Singapore 308900
Phone: +65-6358-2160
Fax: +65-6358-2015
e-mail: singaporesales@powerint.com

JAPAN

Power Integrations, K.K.
Keihin-Tatemono 1st Bldg.
Japan
Phone: +81-45-471-1021
Fax: +81-45-471-3717
e-mail: japansales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

TAIWAN

Power Integrations
International Holdings, Inc.
Taipei, Taiwan
Phone: +886-2-2727-1221
Fax: +886-2-2727-1223
e-mail: taiwansales@powerint.com

INDIA (Technical Support)

Innovatech
Bangalore, India
Phone: +91-80-226-6023
Fax: +91-80-228-9727
e-mail: indiasales@powerint.com

APPLICATIONS FAX

World Wide +1-408-414-9760

